

EC5051 – POWER ELECTRONICS
AND DESIGN
MINI PROJECT

BANDARA H.G.U.N.

2018/E/016

SEMESTER 5

06/02/2022


FACULTY OF ENGINEERING, UNIVERSITY OF JAFFNA
EC5051 – POWER ELECTRONICS AND DESIGN
MINI PROJECT – 2022

DESIGN REQUIREMENTS OF THE DC POWER SUPPLY

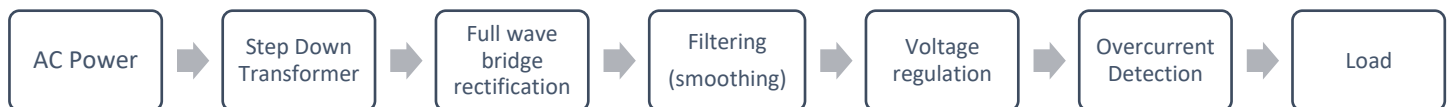- 1) Main supply with switch: 230V, 50Hz
- 2) Over current protection (fuse)
- 3) Dual output
- 4) Operation mode
 - Independent
 - Series
 - Parallel
- 5) Output voltage range: 0-30V
- 6) Output current rate: 0-3A
- 7) Over current indicator

DESIGN CONSIDERATIONS AND CALCULATIONS

- The flow diagram of the Designed power supply is as follows,



- The AC Section requires a switch and Fuse for safety considerations. So that according to the max output current 5A fuse is selected for AC power section.
- For the step Down transformer,

$$\text{Peak primary voltage} = \sqrt{2} * 230 \text{ V} = 325.26 \text{ V}$$

$$\text{Maximum DC voltage} = 30 \text{ V}$$


Average voltage drop through the 3N246 rectifier = 1.15 V (Datasheet), Rounded up = 2V

Ripple voltage = 3V (nearly)

Peak secondary voltage = 30 + 2 + 3 = 35V

Turn ratio of the Transformer = $\frac{N_1}{N_2} = \frac{325}{35}$

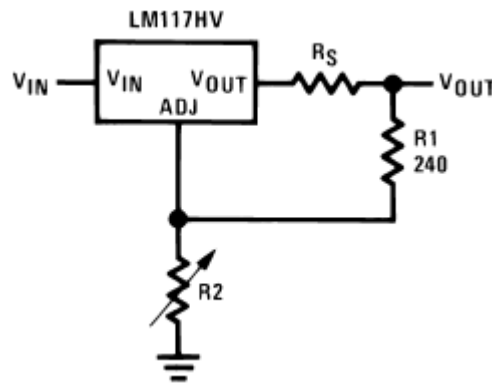- Therefore the turn ratio is selected as 325:25 for the step down transformer.
- For the bridge rectifier, 3N246 Bridge is selected.
- The smoothing capacitor is selected as 2.2mF for better smoothing effect.
- For The Voltage regulator, LM117HVKSTL/883 is selected .



For the calculations of the R1 and R2 (Potentiometer); R1 selected as 450 ohms.

From the datasheet,

$$V_{OUT} = V_{REF} \left(1 + \frac{R2}{R1} \right) + I_{ADJ}R2$$

The IC is designed for a constant $I_{Adj} = 100\mu A$,

So for the max voltage, the equation as follows,

$$30 = 1.25 * \left(1 + \frac{R2}{450} \right) + R2 * 100 * 10^{-6}$$

Solving the equation gives $R2 = 9990 \Omega$ s. So a close - valued Standard valued potentiometer is selected as 10kΩs.

For safety considerations of the IC, Two general purpose 1N4002 Diodes are used for surge current preventions

- For the overcurrent indication, a shunt current monitor circuit for overcurrent detection is used. INA301 current sensing amplifier is used for over current detection and the output of the IC is directly fed to a LED for indication purposes. Pin configurations and calculations for shunt resistor and Limit resistor as follows,
 - V_s is supplied by 4.5 DC voltage(separate)
 - GND is connected to ground
 - RESET is also grounded as stated in the data sheet in order to operate in the transparent condition.
 - As stated in the datasheet the shunt resistor $R_s = 7\text{m}\Omega$, ($I_{\text{max}} = 3.1\text{ A}$, Gain = 20V/V)
 - So the Limiting resistor,

$$RL = (I_{oc} * R_s * \text{gain}) / (80 * 10^{-6})$$

$$RL = (3 * 7/1000 * 20) / (80 * 10^{-6})$$

This gives $RL = 5250\ \Omega$ and a standard valued resistor is selected for RL as $5.23\text{k}\Omega$.

- The Alert pin is kept floating condition and Out pin is connected to the indicator LED.

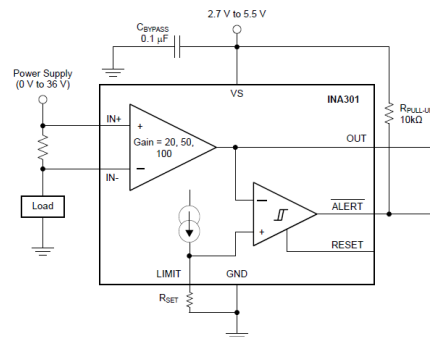


Figure 1: Functional Diagram of the INA301 current sensing amplifier

- Since the Max current of the Power supply doesn't exceed 2.5 A . The Indicator circuit is tested separately. Following are the results of the tests.




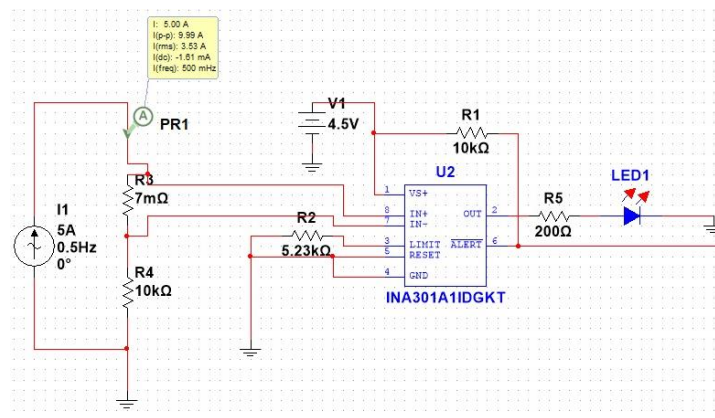
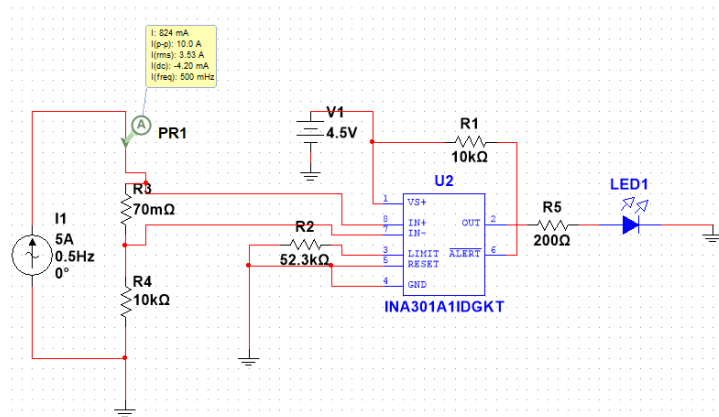


Figure 2: When the current is greater than slightly 3.3 A, The LED is on

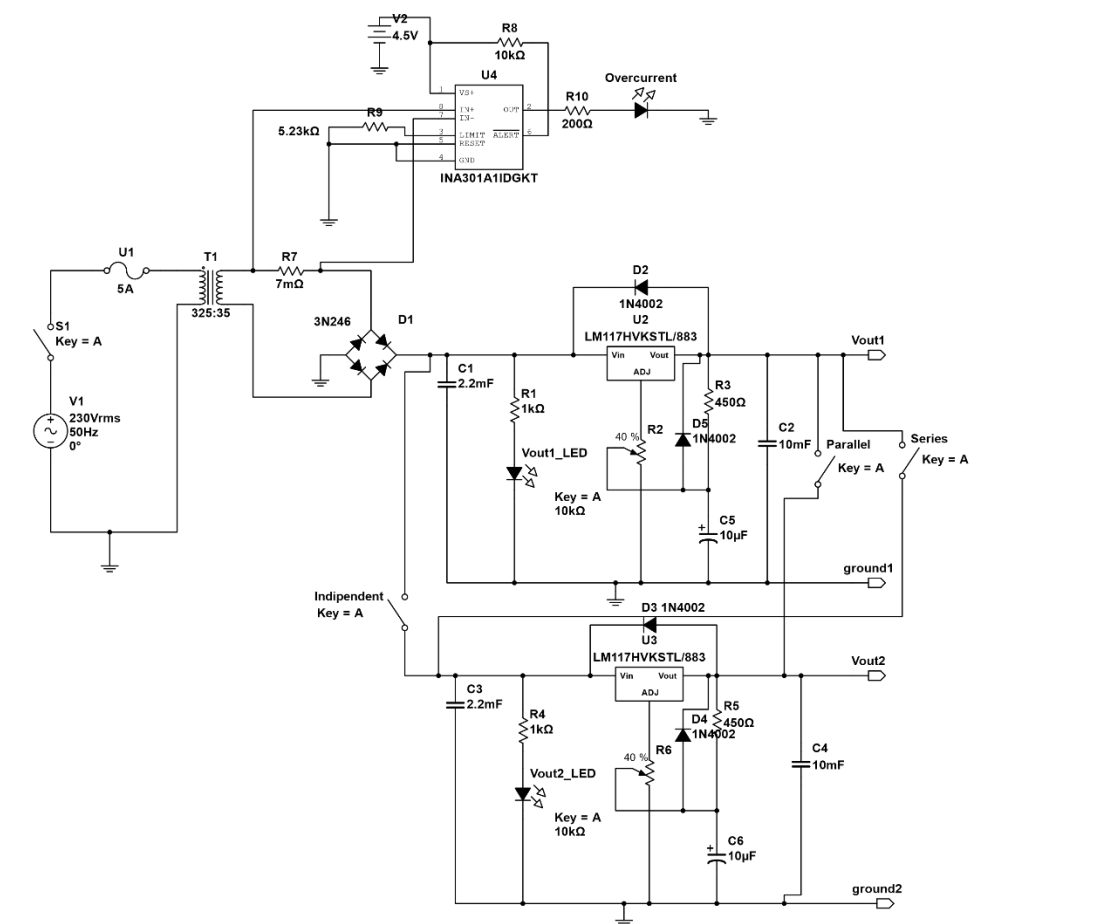

DESIGN SIMULATIONS AND RESULTS

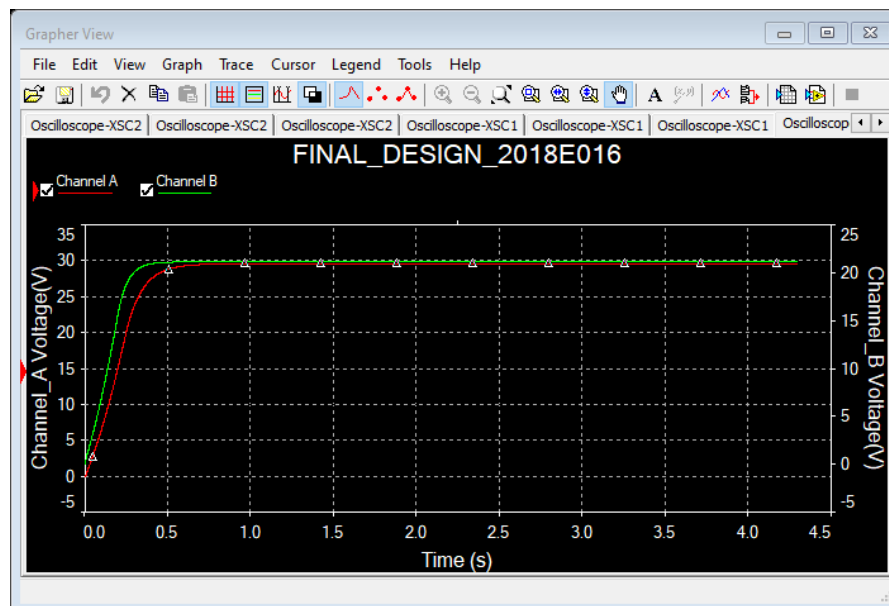

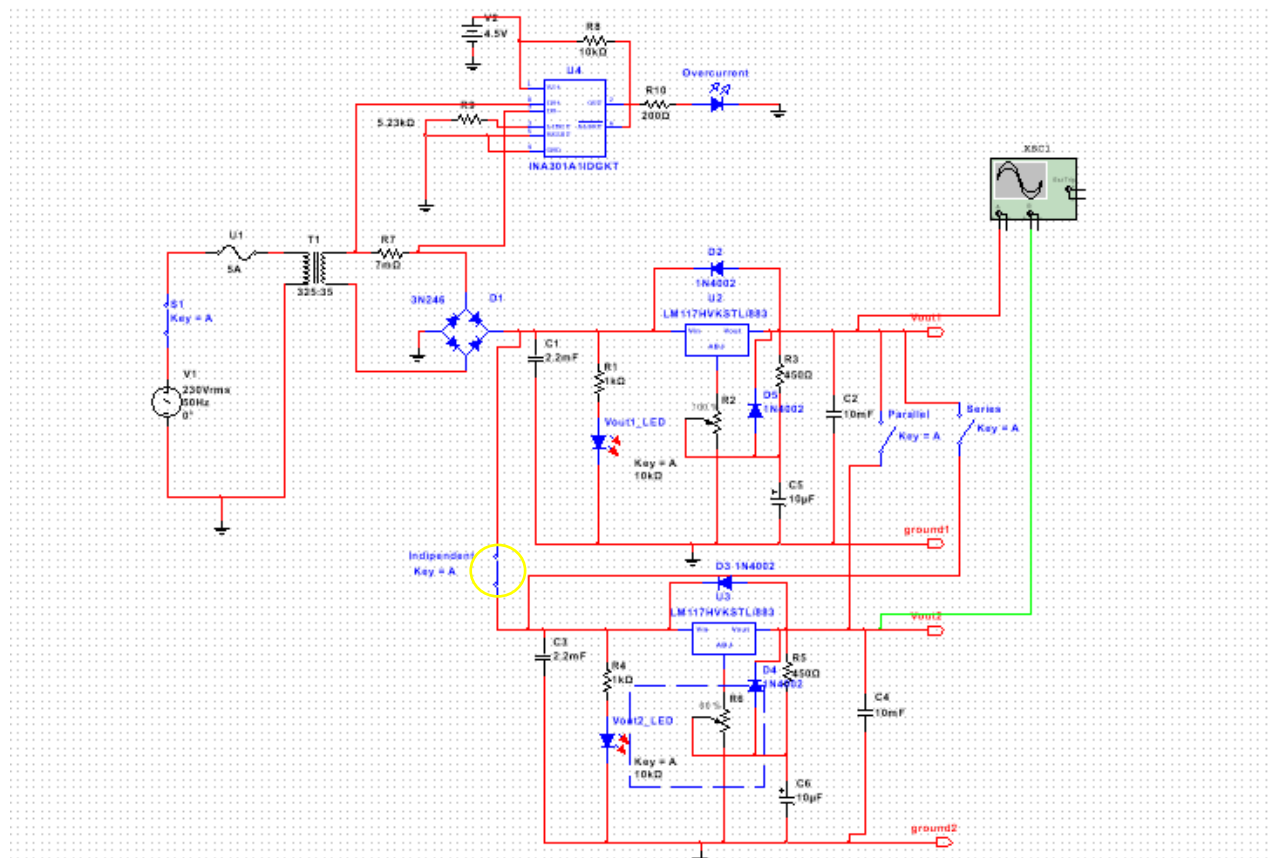

2. PARRALLEL OPERATION MODE

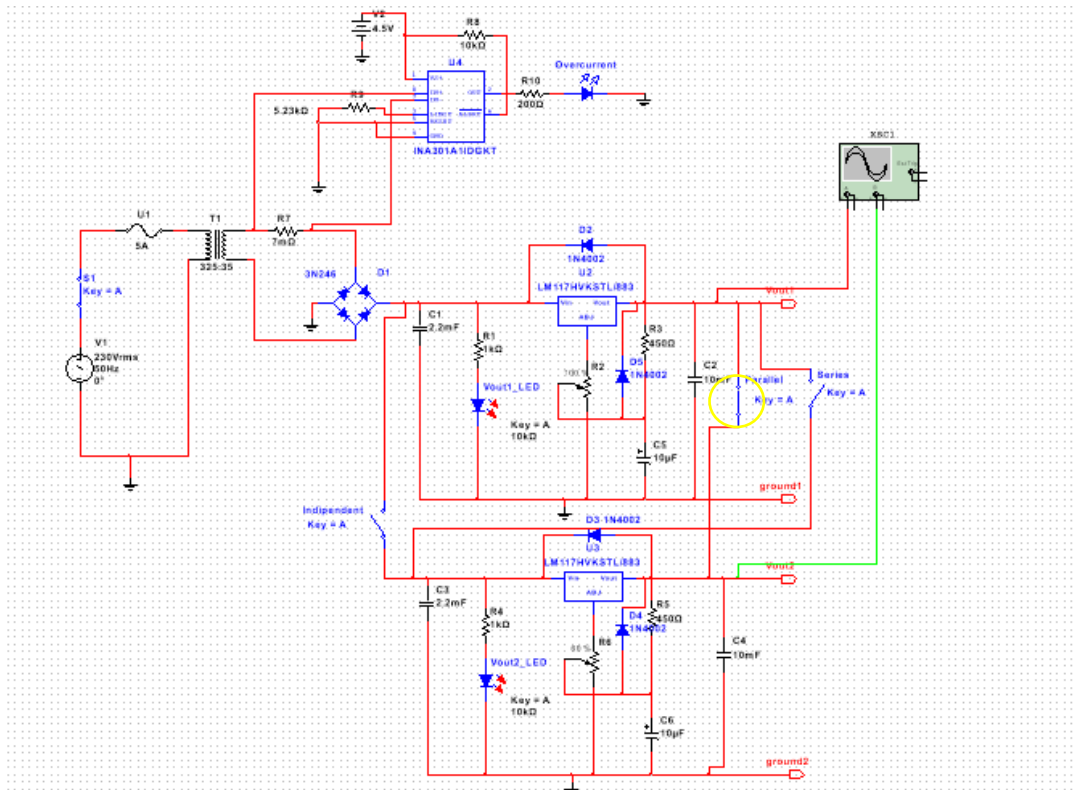


Figure 7: The Circuit on Parallel operation

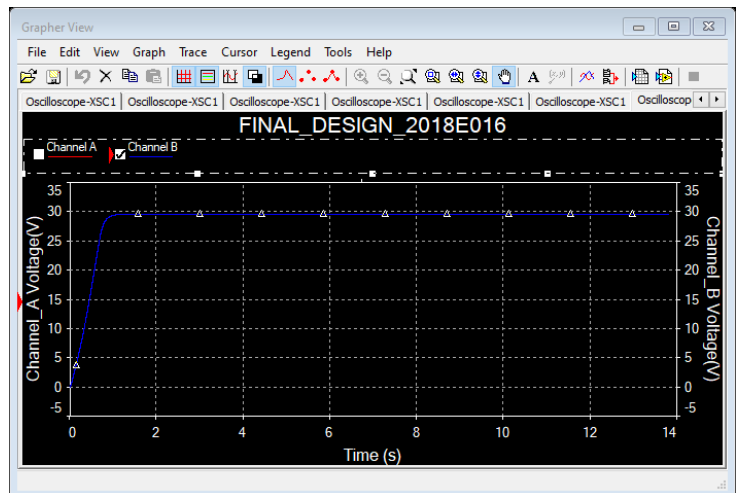
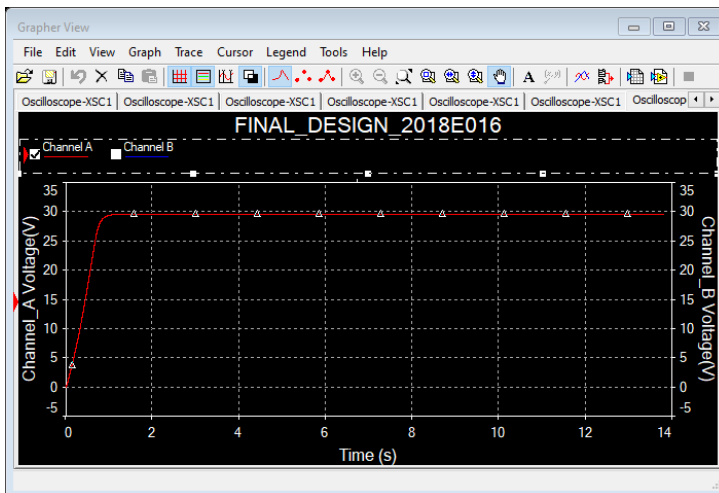


Figure 8: Oscilloscope outputs for the parallel operation

3. SERIES OPERATION MODE

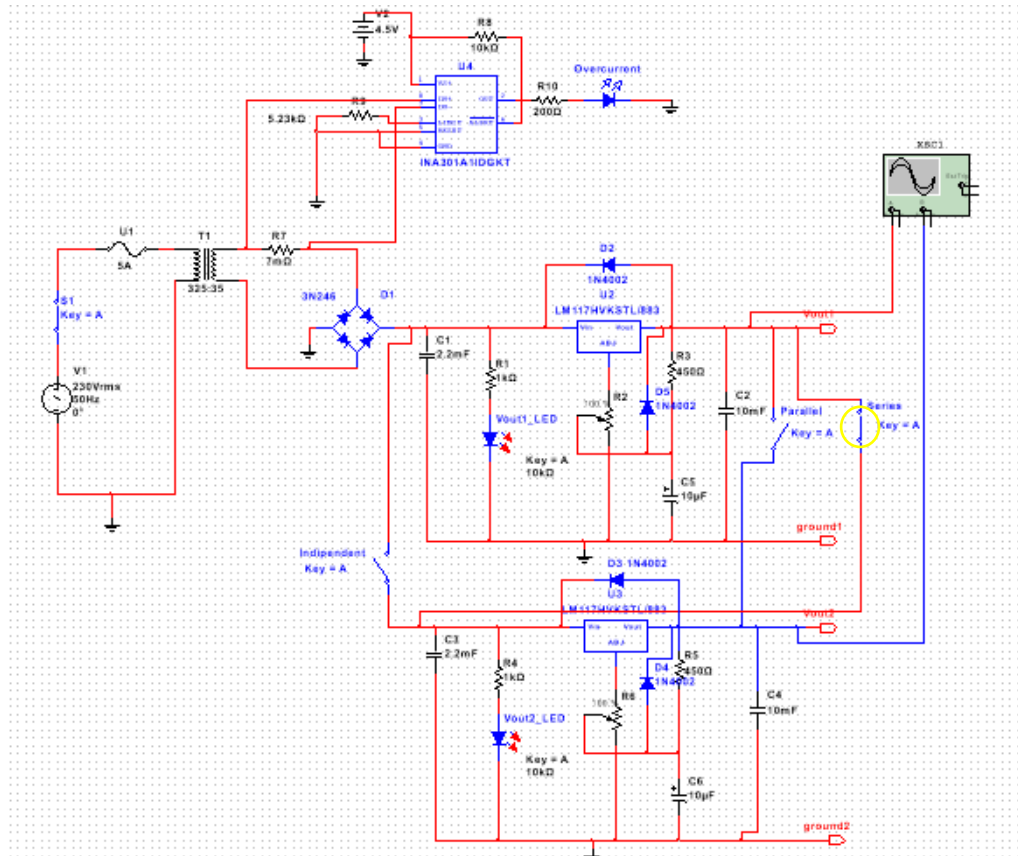


Figure 9: Series operation of the circuit

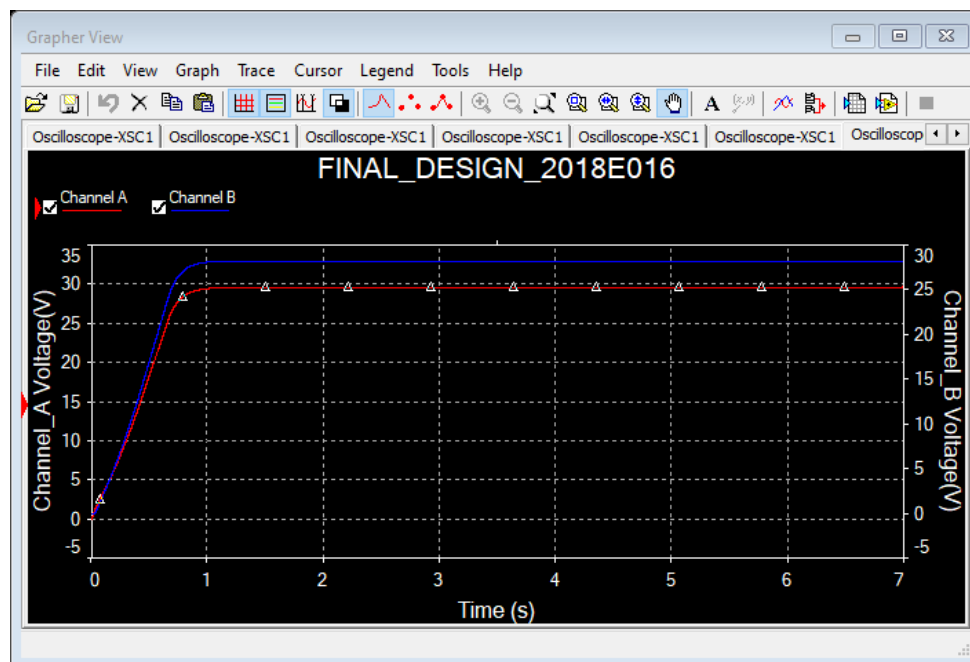


Figure 10: Oscilloscope output for the series operation